


PHYS 1220 Mid-Term Exam 2

November 3rd, 2016

1) An electron moving in the direction of the $+x$ -axis enters a magnetic field. If the electron experiences a magnetic deflection in the $-y$ direction, the direction of the magnetic field in this region points in the direction of the


- A) $-y$ -axis. B) $+z$ -axis. C) $+y$ -axis. D) $-z$ -axis. E) $-x$ -axis.

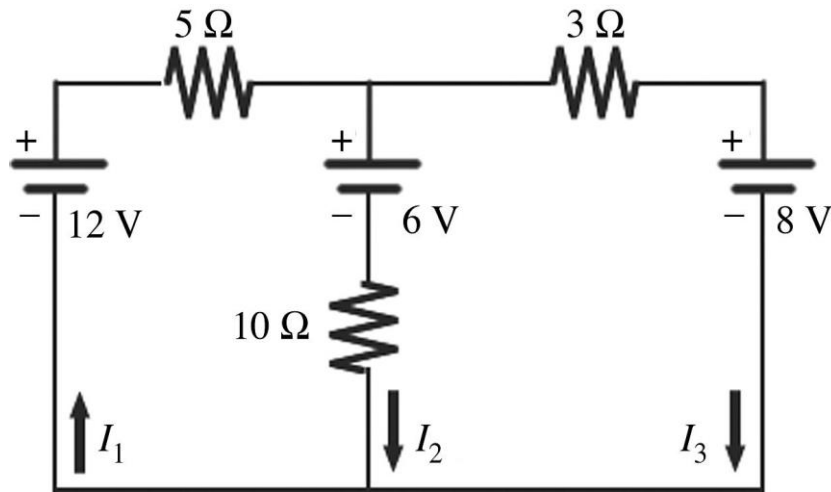2) For the circuit shown in the figure, all quantities are accurate to 2 significant figures. What is the value of the current I_1 ?



- A) 0.89 A B) 0.32 A C) 0.11 A D) 0.61 A E) 0.29 A

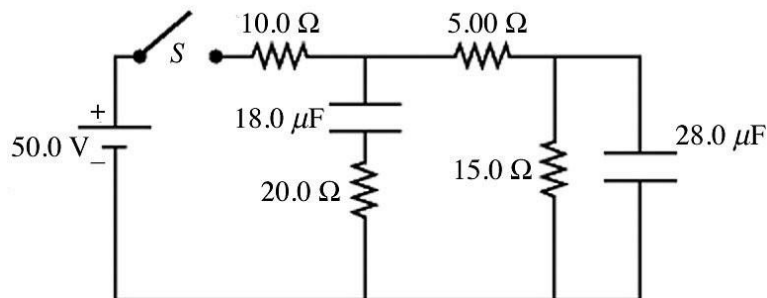3) For the circuit shown in the figure, the capacitors are all initially uncharged, the connecting leads have no resistance, the battery has no appreciable internal resistance, and the switch S is originally open.




After the switch S has been closed for a very long time, what is the potential difference across the $28.0\text{-}\mu\text{F}$ capacitor?

- A) 0.00 V B) 25.0 V C) 3.33 V D) 37.5 V E) 50.0 V

4) You are given a copper bar of dimensions $3\text{ cm} \times 5\text{ cm} \times 8\text{ cm}$ and asked to attach leads to it in order to make a resistor. If you want to achieve the SMALLEST possible resistance, you should attach the leads to the opposite faces that measure

- A) $3\text{ cm} \times 5\text{ cm}$.
- B) $3\text{ cm} \times 8\text{ cm}$.
- C) $5\text{ cm} \times 8\text{ cm}$.
- D) Any pair of faces produces the same resistance.

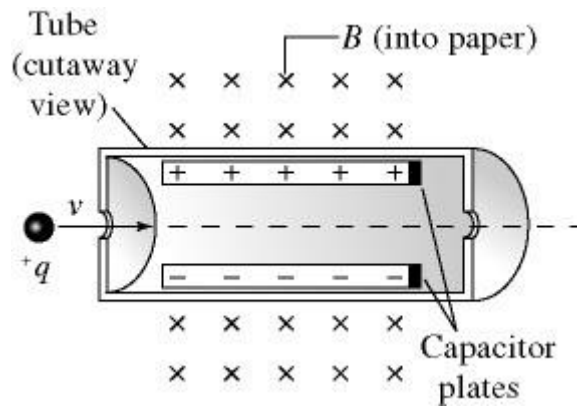5) The figure shows a velocity selector that can be used to measure the speed of a charged particle. A beam of particles is directed along the axis of the instrument. A parallel plate capacitor sets up an electric field E , which is oriented perpendicular to a uniform magnetic field B . If the plates are separated by 2.0 mm and the value of the magnetic field is 0.60 T , what voltage between the plates will allow particles of speed $5.0 \times 10^5\text{ m/s}$ to pass straight through without deflection?




- A) 1900 V
- B) 190 V
- C) 94 V
- D) 3800 V
- E) 600 V

6) Nichrome wire, often used for heating elements, has resistivity of $1.0 \times 10^{-6}\ \Omega \cdot \text{m}$ at room temperature. What length of No. 30 wire (of diameter 0.250 mm) is needed to wind a resistor that has 50 ohms at room temperature?


- A) 22.4 m
- B) 0.61 m
- C) 3.66 m
- D) 6.54 m
- E) 2.45 m

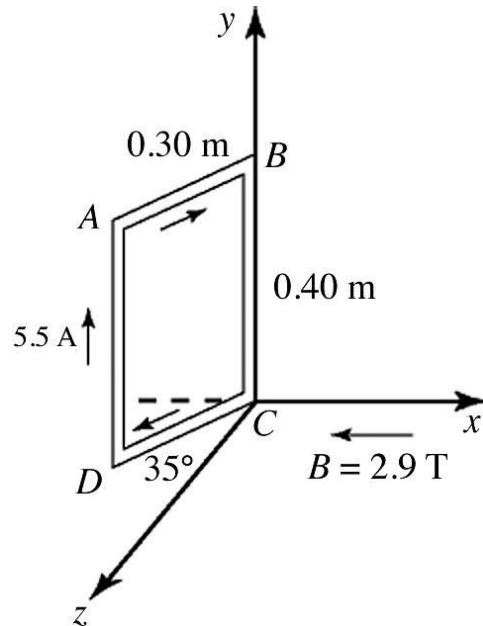7) A rigid rectangular loop, which measures 0.30 m by 0.40 m, carries a current of 5.5 A, as shown in the figure. A uniform external magnetic field of magnitude 2.9 T in the negative x direction is present. Segment CD is in the xz -plane and forms a 35° angle with the z -axis, as shown. Find the magnitude of the external torque needed to keep the loop in static equilibrium.




- A) $1.1 \text{ N} \cdot \text{m}$ B) $1.4 \text{ N} \cdot \text{m}$ C) $1.6 \text{ N} \cdot \text{m}$ D) $0.73 \text{ N} \cdot \text{m}$ E) $1.3 \text{ N} \cdot \text{m}$

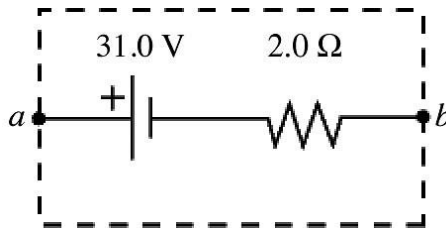8) The emf and the internal resistance of a battery are as shown in the figure. When the terminal voltage V_{ab} is equal to 17.4 V, what is the current through the battery, including its direction?



- A) 8.7 A, from b to a
 B) 6.8 A, from b to a
 C) 16 A, from b to a
 D) 6.8 A, from a to b
 E) 8.7 A, from a to b

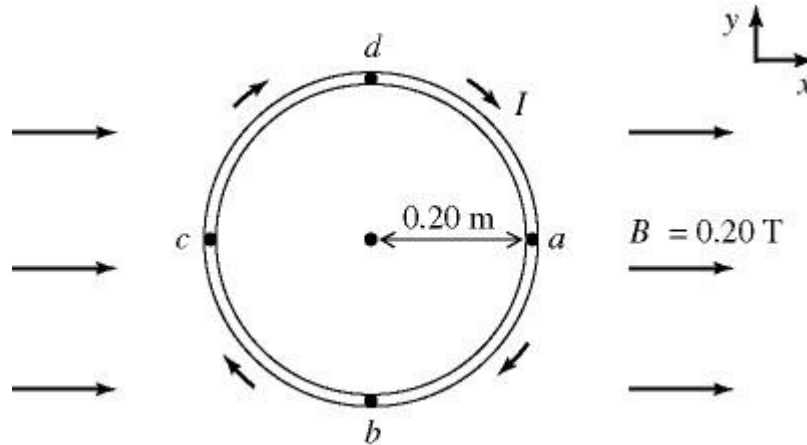9) A rigid circular loop has a radius of 0.20 m and is in the xy -plane. A clockwise current I is carried by the loop, as shown. The magnitude of the magnetic moment of the loop is $0.75 \text{ A}\cdot\text{m}^2$. A uniform external magnetic field, $B = 0.20 \text{ T}$ in the positive x -direction, is present. An external torque changes the orientation of the loop from one of lowest potential energy to one of highest potential energy. The work done by this external torque is closest to




- A) 0.40 J. B) 0.60 J C) 0.30 J. D) 0.20 J. E) 0.50 J.

10) A narrow copper wire of length L and radius b is attached to a wide copper wire of length L and radius $2b$, forming one long wire of length $2L$. This long wire is attached to a battery, and a current is flowing through it. If the electric field in the narrow wire is E , the electric field in the wide wire is


- A) E . B) $2E$. C) $E/2$. D) $E/4$. E) $4E$.

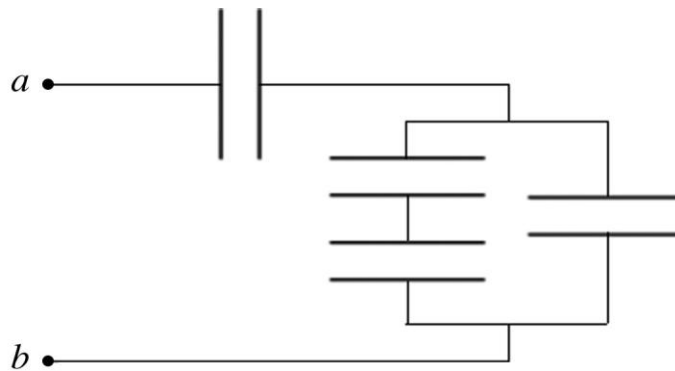11) The capacitors in the network shown in the figure all have a capacitance of $5.0 \mu\text{F}$. What is the equivalent capacitance, C_{ab} , of this capacitor network?



- A) $10 \mu\text{F}$ B) $20 \mu\text{F}$ C) $5.0 \mu\text{F}$ D) $1.0 \mu\text{F}$ E) $3.0 \mu\text{F}$

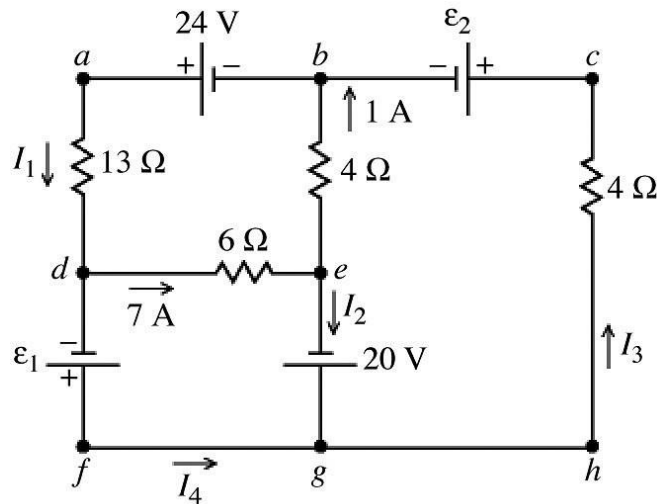12) A multi-loop circuit is shown in the figure. **It is not necessary to solve the entire circuit.** The current I_2 is closest to:




- A) zero. B) 6 A. C) -6 A. D) 8 A. E) -8 A.

13) A $4.0\text{-}\mu\text{F}$ capacitor that is initially uncharged is connected in series with a $4.0\text{-k}\Omega$ resistor and an ideal 17.0-V battery. How much energy is stored in the capacitor 17 ms after the battery has been connected?

- A) $15,000\text{ kJ}$ B) 890 nJ C) $250,000\text{ nJ}$ D) $25\text{ }\mu\text{J}$

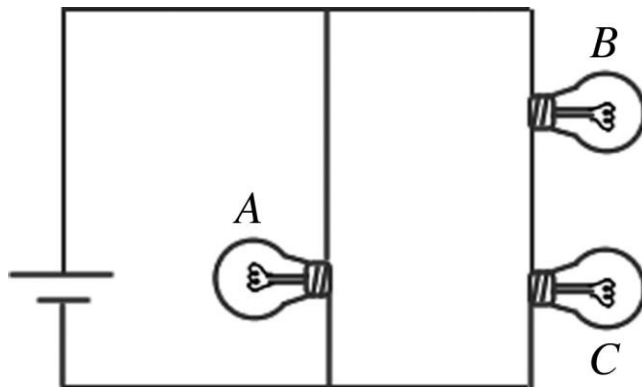14) In the circuit shown in the figure, all the lightbulbs are identical. Which of the following is the correct ranking of the brightness of the bulbs?



- A) A and B have equal brightness, and C is the dimmest.
 B) B and C have equal brightness, and A is the dimmest.
 C) A is brightest, C is dimmest, and B is in between.
 D) A is the brightest, and B and C have equal brightness but less than A .
 E) All three bulbs have the same brightness.


15) The resistivity of gold is $2.44 \times 10^{-8} \Omega \cdot \text{m}$ at room temperature. A gold wire that is 1.8 mm in diameter and 11 cm long carries a current of 170 mA. How much power is dissipated in the wire?

- A) 0.025 mW B) 0.013 mW C) 0.019 mW D) 0.030 mW E) 0.0076 mW

16) If the current density in a wire of radius R is given by $J = kr$, $0 < r < R$, what is the current in the wire?


- A) kR^2 B) $kR^2/2$ C) $3\pi kR^3/2$ D) $kR^3/3$ E) $2\pi kR^3/3$

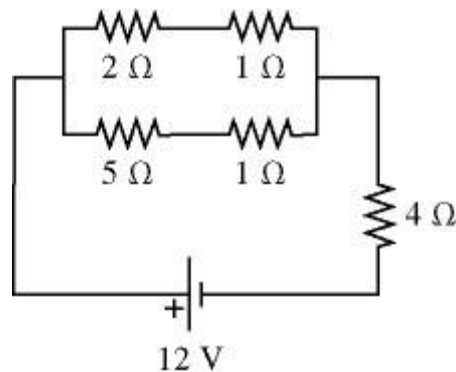17) For the circuit shown in the figure, all quantities are accurate to 3 significant figures. What is the power dissipated in the 2- Ω resistor?




- A) 3.56 W B) 2.67 W C) 8.0 W D) 6.67 W E) 5.33 W

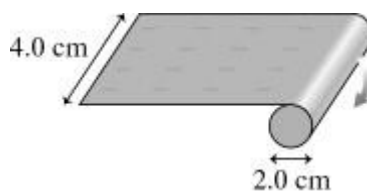18) The figure shows a 2.0-cm diameter roller that turns at 90 rpm. A 4.0-cm wide plastic film is being wrapped onto the roller, and this plastic carries an excess electric charge having a uniform surface charge density of 5.0 nC/cm^2 . What is the current of the moving film?



- A) 23 μA B) 11 μA C) 30 nA D) 190 nA E) 300 nA

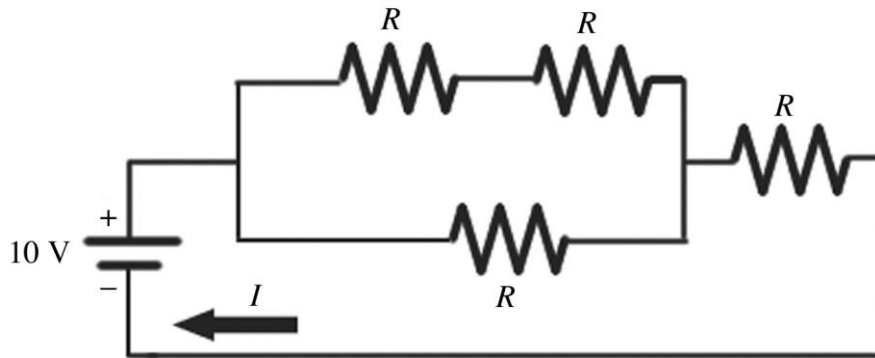19) When four identical resistors are connected to an ideal battery of voltage $V = 10 \text{ V}$ as shown in the figure, the current I is equal to 0.20 A . What is the value of the resistance R of the resistors?



- A) 30Ω B) 10Ω C) 20Ω D) 50Ω E) 40Ω


20) An electron has an initial velocity of $\vec{v} = v_1\hat{x} + v_2\hat{z}$ moving in a magnetic field B_0 oriented in the \hat{x} -direction. What is the motion of the electron due to the magnetic field?

- A) Helical motion starting with $-\hat{y}$ movement
 B) Helical motion starting with $+\hat{y}$ movement
 C) Circular motion starting with $-\hat{y}$ movement
 D) Circular motion starting with $+\hat{y}$ movement
 E) Continuous trajectory in the $-\hat{y}$ direction
 F) Continuous trajectory in the $+\hat{y}$ direction

21) A thin copper rod that is 1.0 m long and has a mass of 0.050 kg is in a magnetic field of 0.10 T . What minimum current in the rod is needed in order for the magnetic force to cancel the weight of the rod?

- A) 4.9 A B) 2.5 A C) 7.6 A D) 1.2 A E) 9.8 A

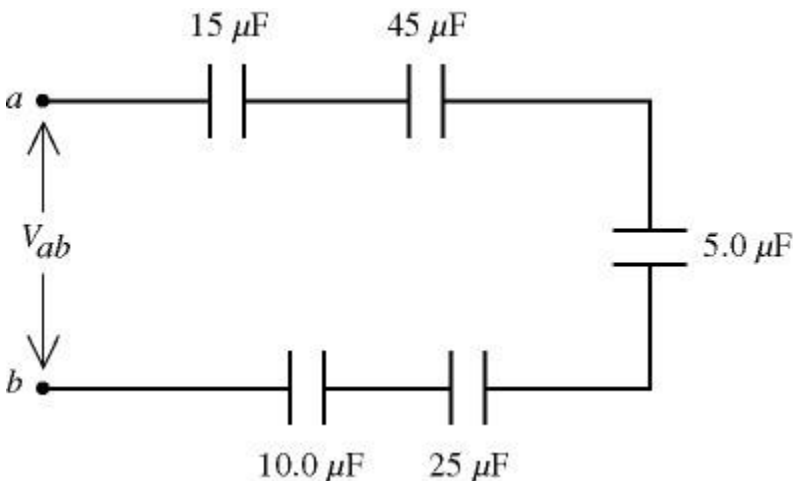22) Five capacitors are connected across a potential difference V_{ab} as shown in the figure. Because of the dielectrics used, each capacitor will break down if the potential across it exceeds 30.0 V . The largest that V_{ab} can be without damaging any of the capacitors is closest to:



- A) 6.0 V .
 B) 30 V .
 C) 150 V .
 D) 580 V .
 E) 64 V .

23) An ideal air-filled parallel-plate capacitor has round plates and carries a fixed amount of equal but opposite charge on its plates. All the geometric parameters of the capacitor (plate diameter and plate separation) are now DOUBLED. If the original capacitance was C_0 , what is the new capacitance?

- A) $C_0/2$ B) $2C_0$ C) C_0 D) $4C_0$ E) $C_0/4$


24) A circular loop of diameter 10 cm, carrying a current of 0.20 A, is placed inside a magnetic field $\vec{B} = 0.30 \text{ T } \hat{k}$. The normal to the loop is parallel to a unit vector $\hat{n} = -0.60\hat{i} - 0.80\hat{j}$. Calculate the magnitude of the torque on the loop due to the magnetic field.

- A) zero B) $0.60 \times 10^{-4} \text{ N} \cdot \text{m}$ C) $1.2 \times 10^{-4} \text{ N} \cdot \text{m}$ D) $4.7 \times 10^{-4} \text{ N} \cdot \text{m}$ E) $2.8 \times 10^{-4} \text{ N} \cdot \text{m}$

25) Each plate of a parallel-plate air-filled capacitor has an area of 0.0020 m^2 , and the separation of the plates is 0.020 mm. An electric field of $3.9 \times 10^6 \text{ V/m}$ is present between the plates. What is the surface charge density on the plates?


- A) $87 \text{ } \mu\text{C/m}^2$ B) $35 \text{ } \mu\text{C/m}^2$ C) $73 \text{ } \mu\text{C/m}^2$ D) $52 \text{ } \mu\text{C/m}^2$ E) $17 \text{ } \mu\text{C/m}^2$

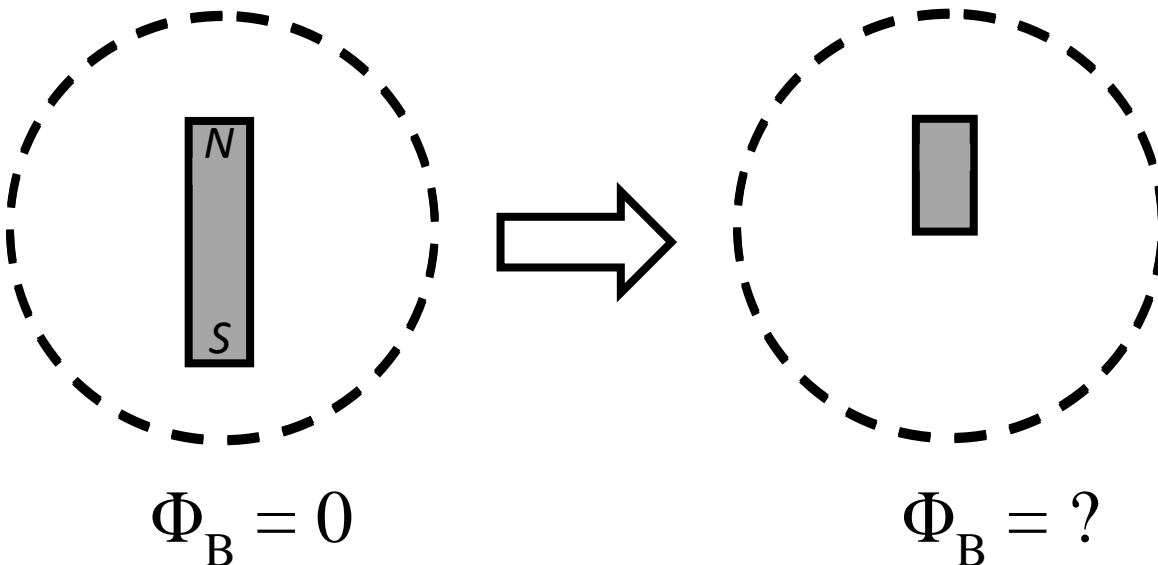26) We initially have the bar magnet on the left side of the figure. We draw a spherical Gaussian surface around that bar magnet and find that the flux, Φ_B , is zero through that Gaussian surface. All of a sudden, the bottom half of the magnet breaks apart. What happens to the flux through that same surface?




- A) Increases B) Decreases C) Stays the same

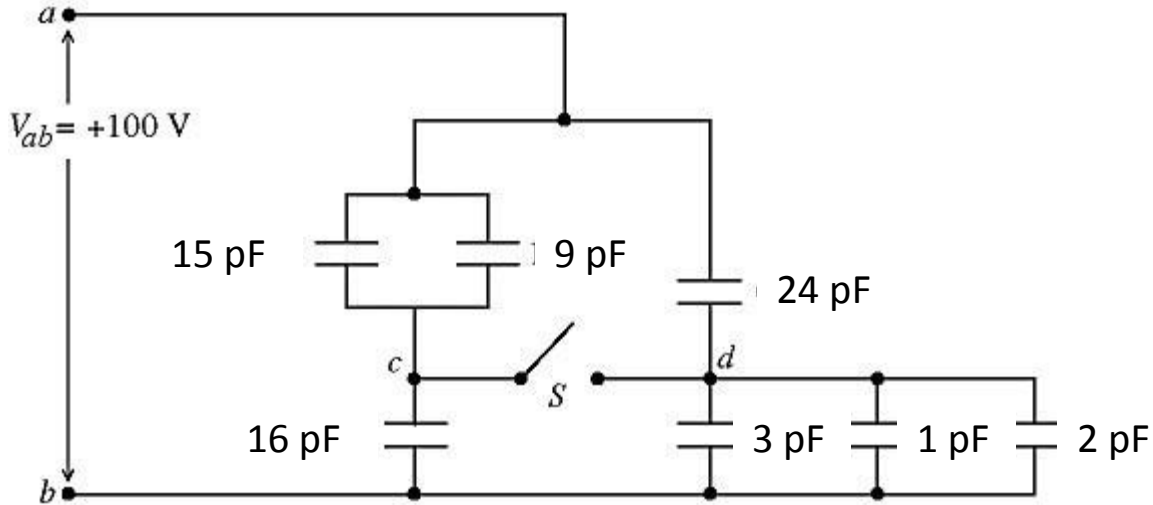27) Initially uncharged capacitors form the capacitive network shown below. A potential difference, $V_{ab} = +100 \text{ V}$, is applied across the network with the switch, S , left open. What is the potential difference V_{cd} across the open switch, S ?



- A) 20 V B) -20 V C) 40 V D) -40 V E) 60 V

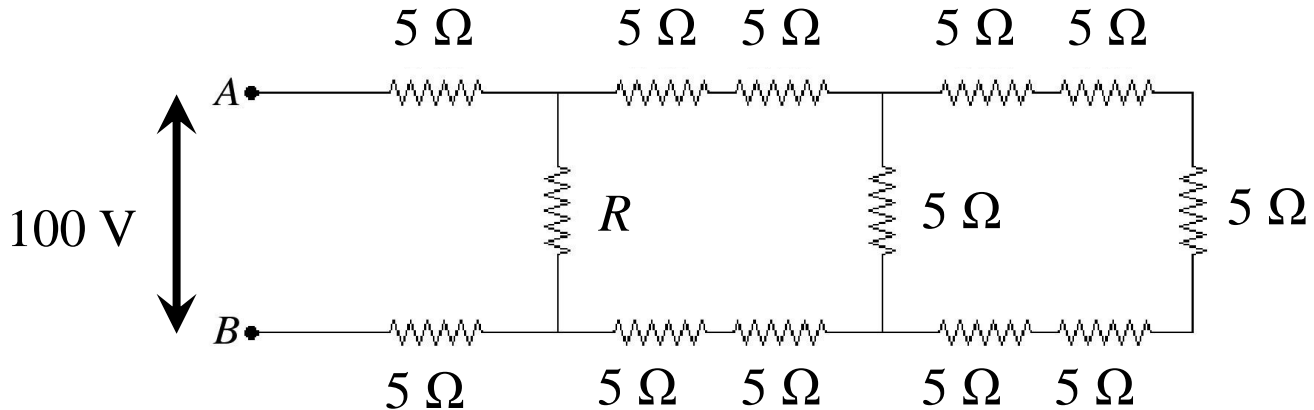28) A resistor network, as seen below, is assembled. A 100 V potential difference is applied between terminals A and B. What value of R is required for 8.44 A to flow between A and B?



- A) 10 Ω B) 5 Ω C) 3 Ω D) 2 Ω E) 1 Ω

29) We have a $\frac{1}{4} \text{ W}$ resistor hooked up to a battery at temperature, T_0 . We apply 10 V across this resistor at this temperature, such that the amount of power dissipation is exactly $\frac{1}{4} \text{ W}$. Next, we dunk this resistor into liquid nitrogen, which drops to the temperature to $T_1 = T_0/2$. If resistance scales as T^2 , how much voltage can we apply when R is at T_1 without damaging the resistor (i.e., exceeding $\frac{1}{4} \text{ W}$)?

- A) 1 V B) 2.5 V C) 5 V D) 20 V E) 40 V

$$e = 1.60 * 10^{-19} \text{ C}$$

$$m_e = 9.11 * 10^{-31} \text{ kg}$$

$$\epsilon_0 = 8.85 * 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$$

$$\oiint \vec{E} \cdot d\vec{A} = \frac{1}{\epsilon} Q_{\text{free}}^{\text{enclosed}}, \text{ where } \epsilon = K\epsilon_0$$

$$Q = CV$$

$$U = \frac{Q^2}{2C} = \frac{1}{2}CV^2 = \frac{1}{2}QV$$

$$\vec{J} = nq\vec{v}_d$$

$$V = IR$$

$$\vec{E} = \rho\vec{J}$$

$$R = \frac{\rho L}{A}$$

$$P = I^2R$$

$$\vec{F} = q \left(\vec{E} + \vec{v} \times \vec{B} \right)$$

$$\Phi_B = \iint \vec{B} \cdot d\vec{A}$$

$$\oiint \vec{B} \cdot d\vec{A} = 0$$

$$\vec{F} = I \left(\vec{\ell} \times \vec{B} \right)$$

$$\vec{\mu} = I\vec{A}$$

$$\vec{\tau} = \vec{\mu} \times \vec{B}$$

$$U = -\vec{\mu} \cdot \vec{B}$$